

CPE 166 Advanced Logic Design

LAB #4

XAVIER HOWELL


Table of contents

1. Introduction
2. Lab Report
 - 4.2 Microprocessor Data Path Design
 - 4.3 Microprocessor Control Path Design
 - 4.4 Final 4-bit Microprocessor Design
3. Conclusion

Introduction


The purpose of parts 2, 3, and part 4 of Lab 4 is to design a simplified microprocessor. The figure below shows the microprocessor diagram with M0, M1, M2 and Cin inputs, one input SW1 and also clock input. The SW1 serves as asynchronous reset function.
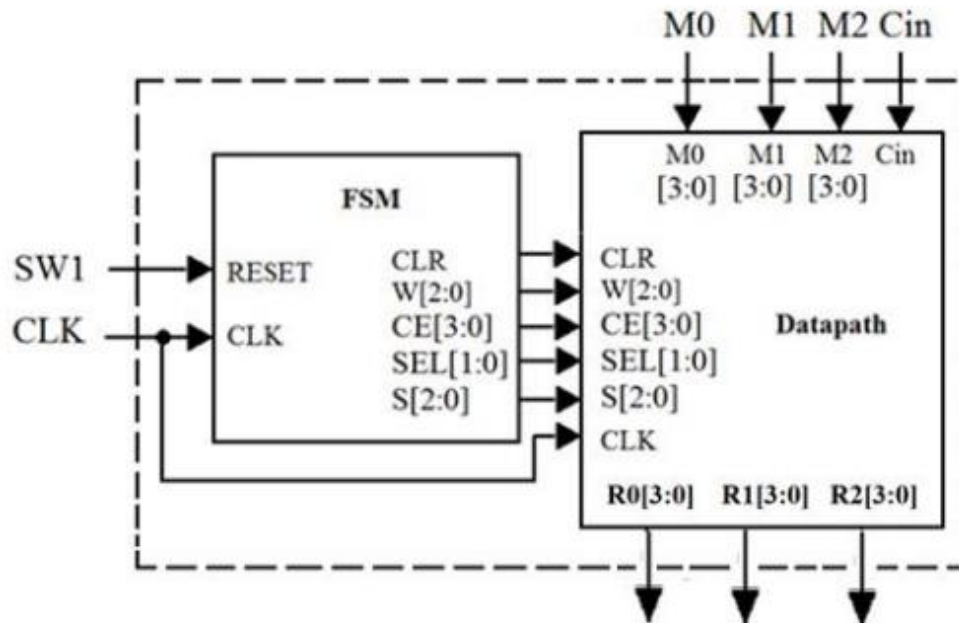
$$R2 = M0 + (\text{not } M1) + \text{Cin}$$



Report

4.2 Design:

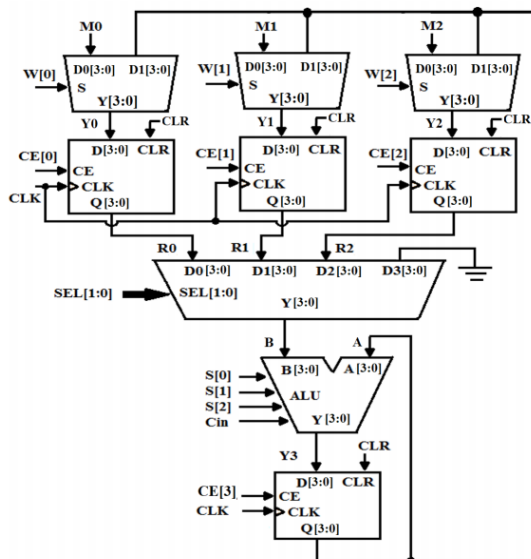

Part two design is of the microprocessor data path. It includes a mux 2 to 1, a mux 4 to 1, alu, and a dffa. I built the hierarchical of this design without simulation of the sub design because I know the parts work.

4.2 VHDL

```
module mux2_1(d0, d1, s, y);
input      [3:0] d0, d1;
input      s;
output     [3:0] y;

reg        [3:0] y;

always@( s or d1 or d0 )
begin
    if (s)
        y = d1;
    else
        y = d0;
end

endmodule
```

```
module mux4_1(d0, d1, d2, d3, sel, y);
input      [3:0] d3, d2, d1, d0;
input      [1:0] sel;
output     [3:0] y;

reg        [3:0] y;

always@( sel or d3 or d2 or d1 or d0 )
begin
    case (sel)
        0 : y = d0;
        1 : y = d1;
        2 : y = d2;
        3 : y = d3;
        //default : y = d0;
    endcase
end

endmodule
```

```
module dffa (d, clr, ce, clk, q);
input      [3:0] d;
input      clr, clk, ce;
output     [3:0] q;

reg        [3:0] q;

always@(posedge clr or posedge clk)
begin
    if(clr) q <= 0;
    else if (ce)
        q <= d;
end

endmodule
```


```
module alu(b, a, s, cin, y);
input      [3:0] b, a;
input      cin;
input      [2:0] s;
output     [3:0] y;

reg        [3:0] y;

always@( s or a or b or cin )
begin
    case (s)
        0 : y = a + b + cin;
        1 : y = a + ~b + cin;
        2 : y = b;
        3 : y = a;
        4 : y = (a & b);
        5 : y = (a | b);
        6 : y = ~a;
        7 : y = (a ^ b);
    endcase
end

endmodule
```

 4.3 Design: Part three is the finite state machine diagram for the “FSM” unit. The FSM is used to implement the control path for the microprocessor. The control path block diagram is shown below.



4.3 VHDL

```

module fsm(clk, rst, clr, sel, w, s, ce);

input clk, rst;
output clr;
output [1:0] sel;
output [2:0] w, s;
output [3:0] ce;

reg clr;
reg [1:0] sel;
reg [2:0] w, s;
reg [3:0] ce;

parameter s0 = 0, s1 = 1, s2 = 2, s3 = 3, s4 = 4, s5 = 5;

reg [2:0] cs, ns;

always@(posedge clk or posedge rst) begin
    if( rst ) begin
        cs <= s0;
    end else begin
        cs <= ns;
    end
end
always@(cs) begin
    case(cs)
        s0 : begin
            clr = 1'b1;
            w = 3'b100;
            s = 3'b010;
            sel = 2'b00;
            ce = 4'b0000;

```

```

        ns <= s1;
    end
    s1 : begin
        clr = 1'b0;
        w = 3'b100;
        s = 3'b010;
        sel = 2'b00;
        ce = 4'b1111;
        ns <= s2;
    end
    s2 : begin
        clr = 1'b0;
        w = 3'b100;
        s = 3'b010;
        sel = 2'b00;
        ce = 4'b1111;
        ns <= s3;
    end
    s3 : begin
        clr = 1'b0;
        w = 3'b100;
        s = 3'b001;
        sel = 2'b01;
        ce = 4'b1111;
        ns <= s4;
    end
    s4 : begin
        clr = 1'b0;
        w = 3'b100;
        s = 3'b001;
        sel = 2'b01;
        ce = 4'b0111;
        ns <= s5;
    end
    s5 : begin
        clr = 1'b0;
        w = 3'b100;
        s = 3'b001;
        sel = 2'b01;
        ce = 4'b0111;
        ns <= s5;
    end
    //default : ns = s0;
endcase
end
endmodule

```

4.4 Design: This part is to complete the design of the top module for the simplified 4-bit microprocessor.

4.4 VHDL

```
module top(rst, clk, m0, m1, m2, cin, r0, r1, r2);

input clk, cin, rst;
input [3:0] m0, m1, m2;
output [3:0] r0, r1, r2;

wire clr;
wire [1:0] sel;
wire [2:0] s, w;
wire [3:0] ce;

fsm fsm1(.clk(clk), .rst(rst), .clr(clr), .sel(sel), .w(w), .s(s), .ce(ce));

datapath datapath1(.clr(clr), .w(w), .ce(ce), .sel(sel), .s(s), .clk(clk), .m0(m0), .m1(m1), .m2(m2), .cin(cin), .r0(r0), .r1(r1), .r2(r2));

endmodule
```

4.4 Testbench

```
module top_tb();

reg clk, rst, cin;
reg [3:0] m0, m1, m2;
wire [3:0] r0, r1, r2;

top uut(.rst(rst), .clk(clk), .m0(m0), .m1(m1), .m2(m2), .cin(cin), .r2(r2), .r0(r0), .r1(r1));

always
begin
#5 clk = ~clk;
end

initial
begin
clk = 0; rst = 1; cin = 1; m0=0; m1=0; m2=0;

#10 m0 = 3; rst = 0;
    m1 = 13;
#150

$stop;
end
endmodule
```

Conclusion

In conclusion the purpose of this lab was to design a simple microprocessor that implemented the logic equation $R2 = M0 + \text{not}(M1) + \text{Cin}$. We used a hierarchical design method which made the lab easier because we have already previously made the modules used in this design earlier.